

Dual Electret Mic → Sabrent USB Audio (CM108) — Stereo Wiring Schematic

MIC1 → Left channel (Tip) | MIC2 → Right channel (Ring) | Sleeve = GND



Notes:

- CM108 stereo ADC → Linux presents as 2-channel capture (Left=MIC1, Right=MIC2).
- MIC1 → Tip (Left), MIC2 → Ring (Right), both (–) → Sleeve (GND).
- CM108 internal mic bias (~2.2 kΩ + ~2.2 V) on each channel; R1/R2 optional.
Verify with DMM: probe Tip vs GND — expect ~1.5–2.2 V DC when USB plugged in.
- C1, C2: 1 μF film (non-polar preferred); if electrolytic, (+) toward mic/bias node.
- C_dec: 0.1 μF ceramic close to each resistor to suppress power-rail noise.
- Use shielded cable from capsule to cap; keep runs < 20 cm; route away from servo wires.
- After wiring: arecord -l → python3 scripts/test_microphone.py → alsamixer to tune gain.